



Learn Git and GitHub without any code!

Using the Hello World guide, you'll start a branch, write comments, and open a pull request.

[Read the guide](#)

[FranciscaCampos](#) / [Digital-electronics-1](#)

[Code](#)

[Issues](#)

[Pull requests](#)

[Actions](#)

[Projects](#)

[Wiki](#)

[Security](#)

[Insights](#)

[Settings](#)

[main](#) ▾



[Digital-electronics-1](#) / [Labs](#) / [05-counter](#) / [README.md](#)



[FranciscaCampos](#) Update README.md



1 contributor

[Raw](#)



[Blame](#)



157 lines (121 sloc) | 4.79 KB

Lab 5: Binary counter

1. Preparation tasks

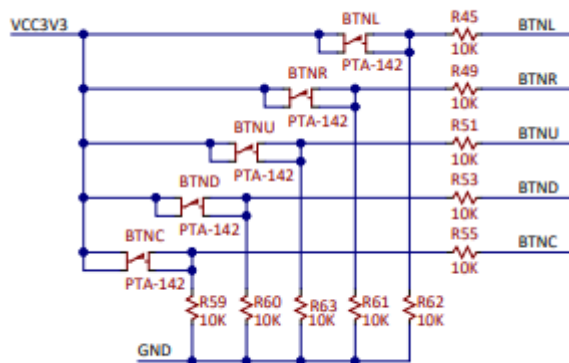 

Time Interval	Number of clk periods	Number of clk periods in hex	Number of clk periods in binary
2 ms	200 000	x"3_0d40"	
b"0011_0000_1101_0100_0000"			
4 ms	400 000	x"6_1A80"	
b"0110_0001_1010_1000_0000"			
10 ms	1 000 000	x"F_4240"	
b"1111_0100_0010_0100_0000"			
250 ms	25 000 000	x"17D_7840"	
b"0001_0111_1101_0111_1000_0100_0000"			
500 ms	50 000 000	x"2FA_F080"	
b"0010_1111_1010_1111_0000_1000_0000"			
1 sec	100 000 000	x"5F5_E100"	
b"0101_1111_0101_1110_0001_0000_0000"			

2. Seven-segment display decoder

```

p_cnt_up_down : process(clk)
begin
    if rising_edge(clk) then

        if (reset = '1') then                -- Synchronous reset
            s_cnt_local <= (others => '0'); -- Clear all bits

        elsif (en_i = '1') then              -- Test if counter is enabled

```

```

        -- TEST COUNTER DIRECTION HERE
        if (cnt_up_i = '1') then
            s_cnt_local <= s_cnt_local + 1;
        else
            s_cnt_local <= s_cnt_local - 1;
        end if;

    end if;
end if;
end process p_cnt_up_down;

-- Output must be retyped from "unsigned" to "std_logic_vector"
cnt_o <= std_logic_vector(s_cnt_local);

p_reset_gen : process
begin
    s_reset <= '0';
    wait for 12 ns;

    -- Reset activated
    s_reset <= '1';
    wait for 73 ns;

    s_reset <= '0';
    wait;
end process p_reset_gen;

-----
-- Data generation process
-----
p_stimulus : process
begin
    report "Stimulus process started" severity note;


    -- Enable counting
    s_en      <= '1';

    -- Change counter direction
    s_cnt_up <= '1';
    wait for 380 ns;
    s_cnt_up <= '0';
    wait for 220 ns;

    -- Disable counting
    s_en      <= '0';

    report "Stimulus process finished" severity note;
    wait;
end process p_stimulus;

```

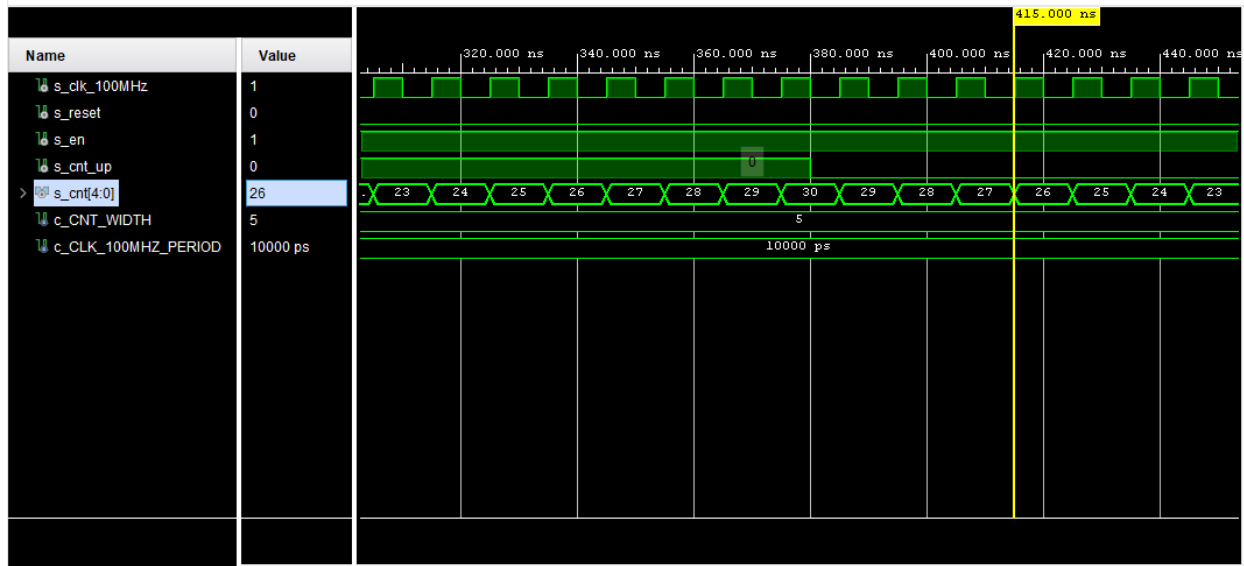

3. Top Level

```

-----
-- Architecture body for top level
-----

```

```

architecture Behavioral of top is

```

```

    -- Internal clock enable

```

```

    signal s_en : std_logic;

```

```

    -- Internal counter

```

```

    signal s_cnt : std_logic_vector(4 - 1 downto 0);

```

```

begin

```

```

-----
-- Instance (copy) of clock_enable entity

```

```

clk_en0 : entity work.clock_enable

```

```

    generic map(

```

```

        g_MAX => g_MAX

```

```

    )

```

```

    port map(

```

```

        --- WRITE YOUR CODE HERE

```

```

        clk    => CLK100MHZ,

```

```

        reset => BTNC,

```

```

        ce_o  => s_en

```

```

    );

```

```

-----
-- Instance (copy) of cnt_up_down entity

```

```

bin_cnt0 : entity work.cnt_up_down

```

```

    generic map(

```

```

        --- WRITE YOUR CODE HERE

```

```

        g_CNT_WIDTH => g_CNT_WIDTH

```

```

    )

```

```

    port map(

```

```

        --- WRITE YOUR CODE HERE

```

```
    clk => CLK100MHZ,
    reset => BTNC,
    en_i => s_en
    cnt_up_i => SW,
    cnt_o => s_cnt
);

-- Display input value on LEDs
LED(3 downto 0) <= s_cnt;

-----

-- Instance (copy) of hex_7seg entity
hex2seg : entity work.hex_7seg
    port map(
        hex_i    => s_cnt,
        seg_o(6) => CA,
        seg_o(5) => CB,
        seg_o(4) => CC,
        seg_o(3) => CD,
        seg_o(2) => CE,
        seg_o(1) => CF,
        seg_o(0) => CG
    );

-- Connect one common anode to 3.3V
AN <= b"1111_1110";

end architecture Behavioral;
```

